


# Physics HW 4 Solutions

## Problem 1:


Write a program to solve for the currents in a resistor cube. There are 12 resistors, one along each edge. A voltage source is connected across a body diagonal of the cube.

- Find the equivalent resistance for the symmetric case when all the resistors have the same resistance, say 1 Ohm. You might remember this problem from freshman E&M.
- Plot the equivalent resistance as a function of one resistor (choose any one) when all 11 others are fixed at 1 Ohm
- How many different cases are there when one resistor is varied as in the previous part?

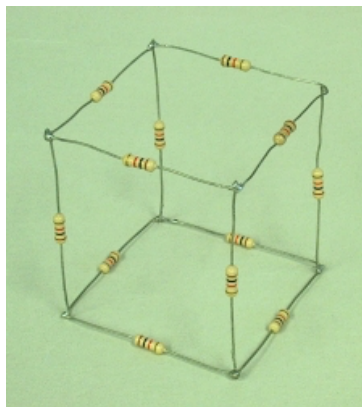
Solution: There are two cases, (a) when you vary a resistor on the edge touching the corner with the voltage applied (call it  $r_1$ ), and (b) when you vary a resistor on an edge that does not touch the corner (call it  $r_6$ ):



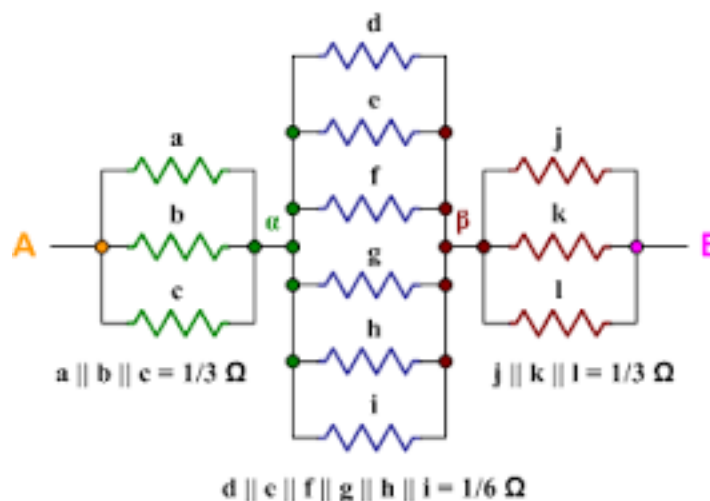This is clear if you look at the equivalent resistor diagram:



So, we vary r1 and r6 in the code and plot:

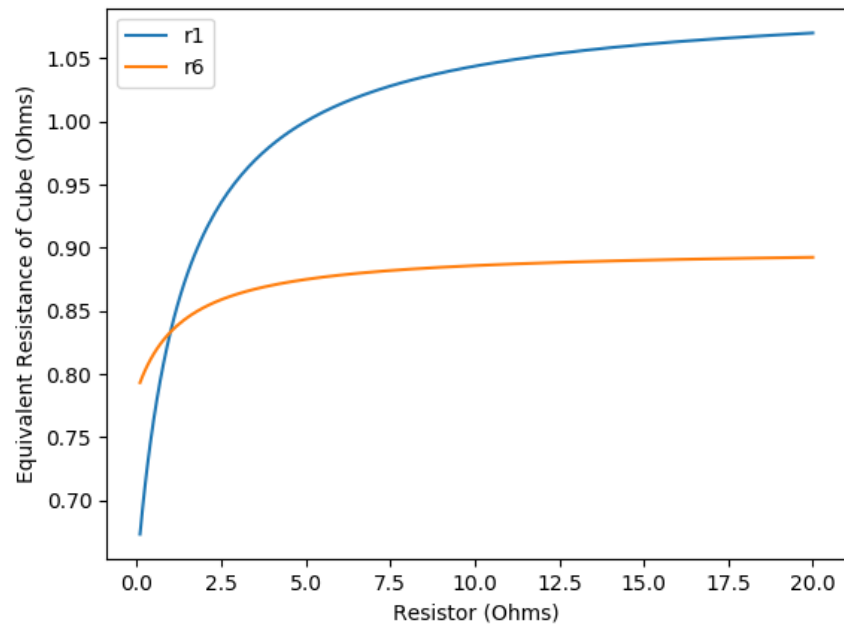

**Problem 2:**

Carbon suboxide is five-atom linear molecule. Simulate a  $C_3O_2$  molecule with a linear system of 5 masses and 4 ideal springs, similar to the linear triatomic molecule. There are two distinct mass values  $M$  and  $m$ , and two distinct force constants  $K$  and  $k$ . Search the web for information on the force constants. If you cannot locate data on  $C_3O_2$ , make a reasonable estimate from data on Molecular Vibrations simpler molecules with similar bonds, for example  $CO_2$ . Find the eigenfrequencies and normal modes for longitudinal oscillations.

Solution: To avoid huge or tiny numbers, we will work in units where the mass is in atomic mass units (AMU) and the strength is in N/cm. The values are then:

$m(\text{oxygen}) = 16$ .

$m(\text{carbon}) = 12$ .

$k_1 = 14.87$

$k_2 = 14.15$

In that case, the matrices are:

$M =$

16.00	0.00	0.00	0.00	0.00
0.00	12.00	0.00	0.00	0.00
0.00	0.00	12.00	0.00	0.00
0.00	0.00	0.00	12.00	0.00
0.00	0.00	0.00	0.00	16.00

$K =$

14.87	-14.87	0.00	0.00	0.00
-14.87	29.02	-14.15	0.00	0.00
0.00	-14.15	28.30	-14.15	0.00
0.00	0.00	-14.15	29.02	-14.87
0.00	0.00	0.00	-14.87	14.87

Performing the eigenvalue solution we get:

Eigenvalues =  
 0.3677531941404121,  
 -8.05768684422316e-17,  
 1.4638859380195373,  
 2.9799551391929215,  
 4.2421557286471305

Eigenvectors =

-0.16	-0.12	0.12	0.08	0.04
-0.09	-0.12	-0.07	-0.18	-0.15
-0.00	-0.12	-0.18	-0.00	0.19
0.09	-0.12	-0.07	0.18	-0.15
0.16	-0.12	0.12	-0.08	0.04

**Problem 3:**

*Repeat Problem 1 for an octahedron.*

Solution: There is only one case that matters here (the others cause no change in the equivalent resistance because they connect points at the same potential):

